
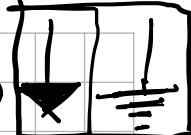


Node Analysis

Ground: \Rightarrow 

* Ultimately KCL. এই ব্যবহার।

Solution Steps:

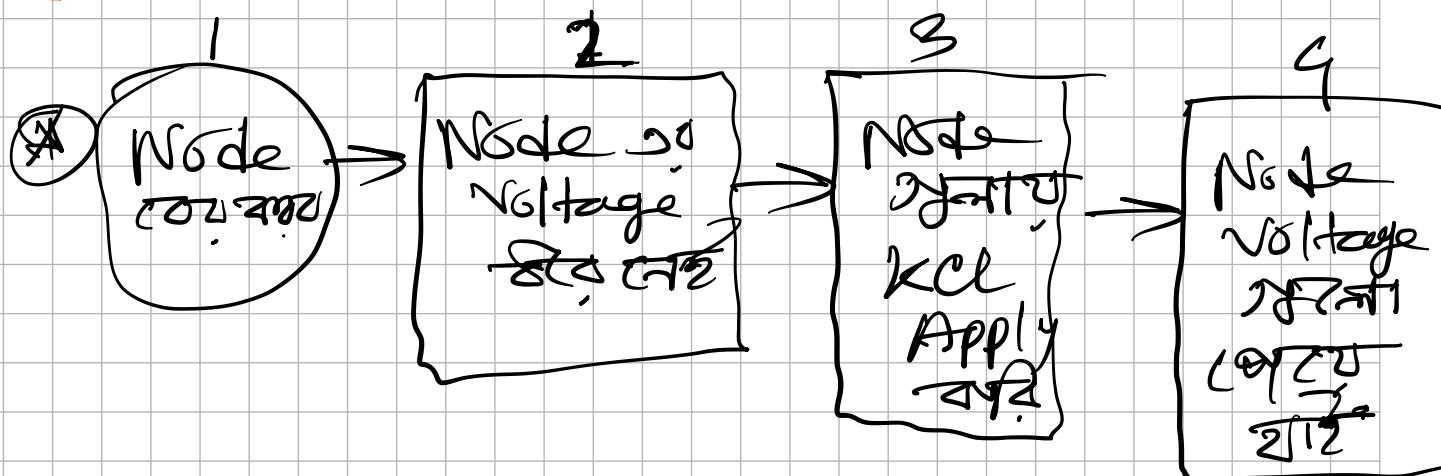

→ অন্তর্ভুক্ত Additionally Ground ভূমিকা।

[প্রতি question এ না প্রয়োজন করা হবে।]


[সম্ভবত Most of the voltage across most of the elements connected to ground।]

সম্ভব

a, node

b, node

c, node

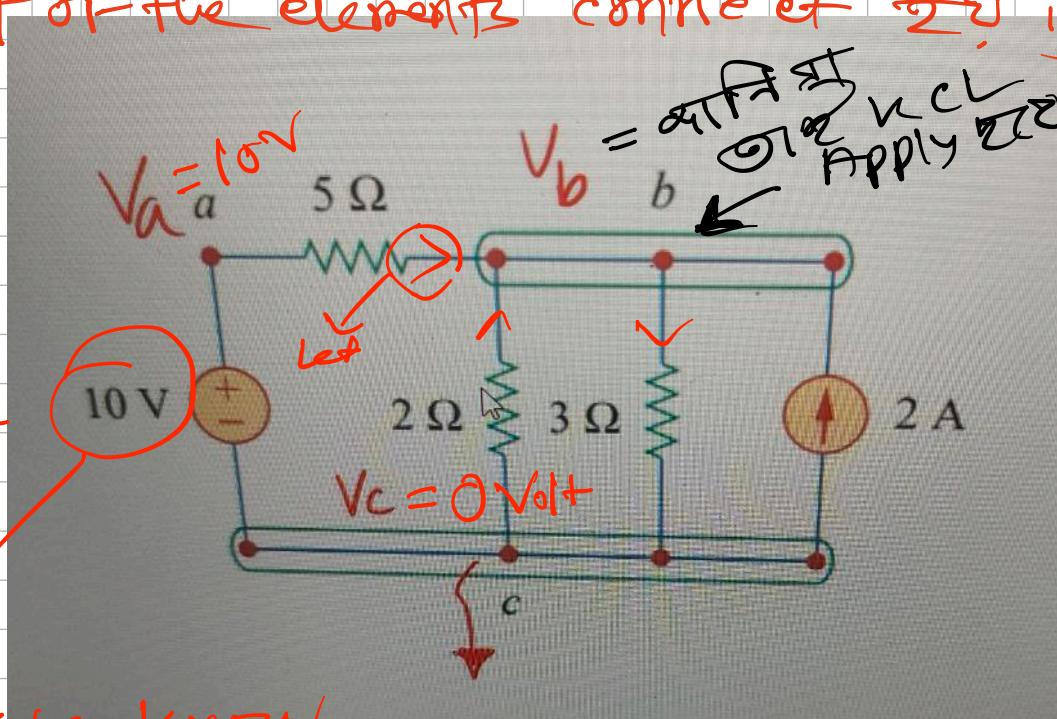

we know

$$V_{ab} = V_a - V_b \Rightarrow 10V = V_a - V_b \Rightarrow V_a - 0 = 10V$$

$$\therefore V_a = 10V$$



Ground node 2nd for op
Voltage zero vce,

KCL at V_b :

$$I_{5-2} + I_{2-2} + 2A = I_{3-2}$$

$$\Rightarrow \frac{V_a - V_b}{5} + \frac{V_c - V_b}{2} + 2 = \frac{V_b - V_c}{3}$$

ISMT
Ja teta
 V_b 0.0.


are known,



$$\therefore I_R = \frac{V_p - V_b}{R}$$

$$\Rightarrow \frac{10 - V_b}{5} + \frac{0 - V_b}{2} + 2 = \frac{V_b - 0}{3}$$

$$\Rightarrow V_b = (?)$$

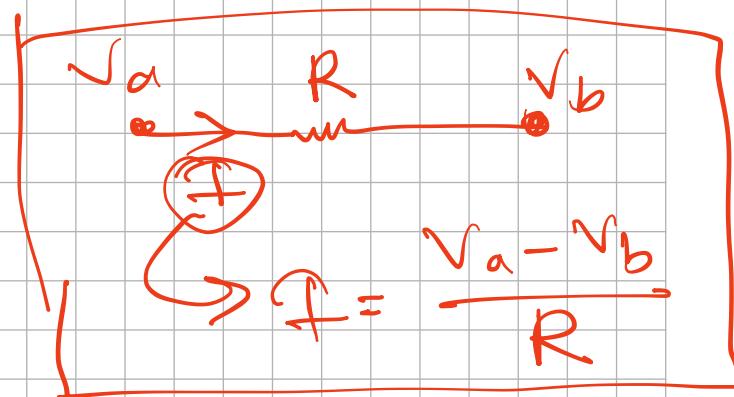

Another Basic:

$$If: V_a \quad V_{ab} \quad V_b$$


$$V_{ab} = V_a - V_b$$

$$\Rightarrow V_a = V_{ab} + V_b$$

$$\Rightarrow V_b = V_{ab} + V_a$$


so

$$0 \quad V_a = ?$$

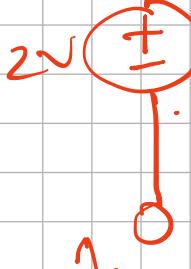

$$\begin{aligned} \text{Here } V_{ab} &= 2V \\ V_b &= 1 \\ V_a &= V_{ab} + V_b \\ &= 2 + 1 \\ &= 3V \end{aligned}$$

Ans

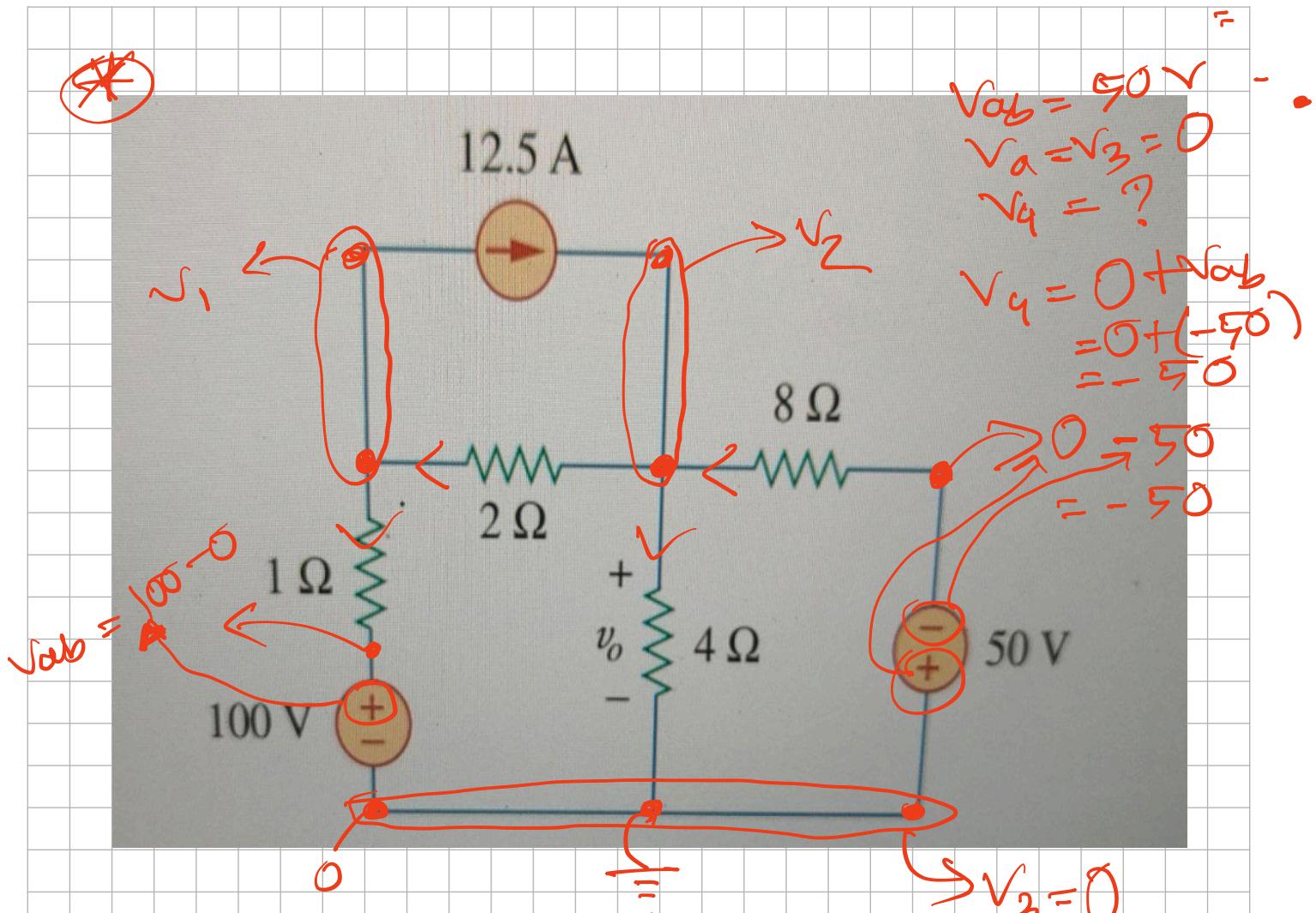

* Node 1 is the ground node.

KCL at V_1 :

$$\frac{\text{V}_2 - \text{V}_1}{2} = \frac{\text{V}_1 - 100}{1} + 12.5$$

$$\Rightarrow \text{V}_2 - \text{V}_1 = 2\text{V}_1 - 200 + 25$$

$$\Rightarrow 3\text{V}_1 - \text{V}_2 = 175$$

KCL at V_2 :

$$12 \cdot 5 + \frac{-50 - V_2}{8} = \frac{V_2 - V_1}{2} + \frac{V_2 - 0}{4}$$


$$\Rightarrow 100 - 50 - V_2 = 4V_2 - 4V_1 + 2V_2$$

$$\Rightarrow -4V_1 + 7V_2 = 50 \quad \text{--- (i)}$$

Solving (i) and (ii): \Rightarrow

$$V_1 = (\quad) \quad \text{and} \quad V_0 = V_2 - 0$$

$$V_2 = (\quad)$$

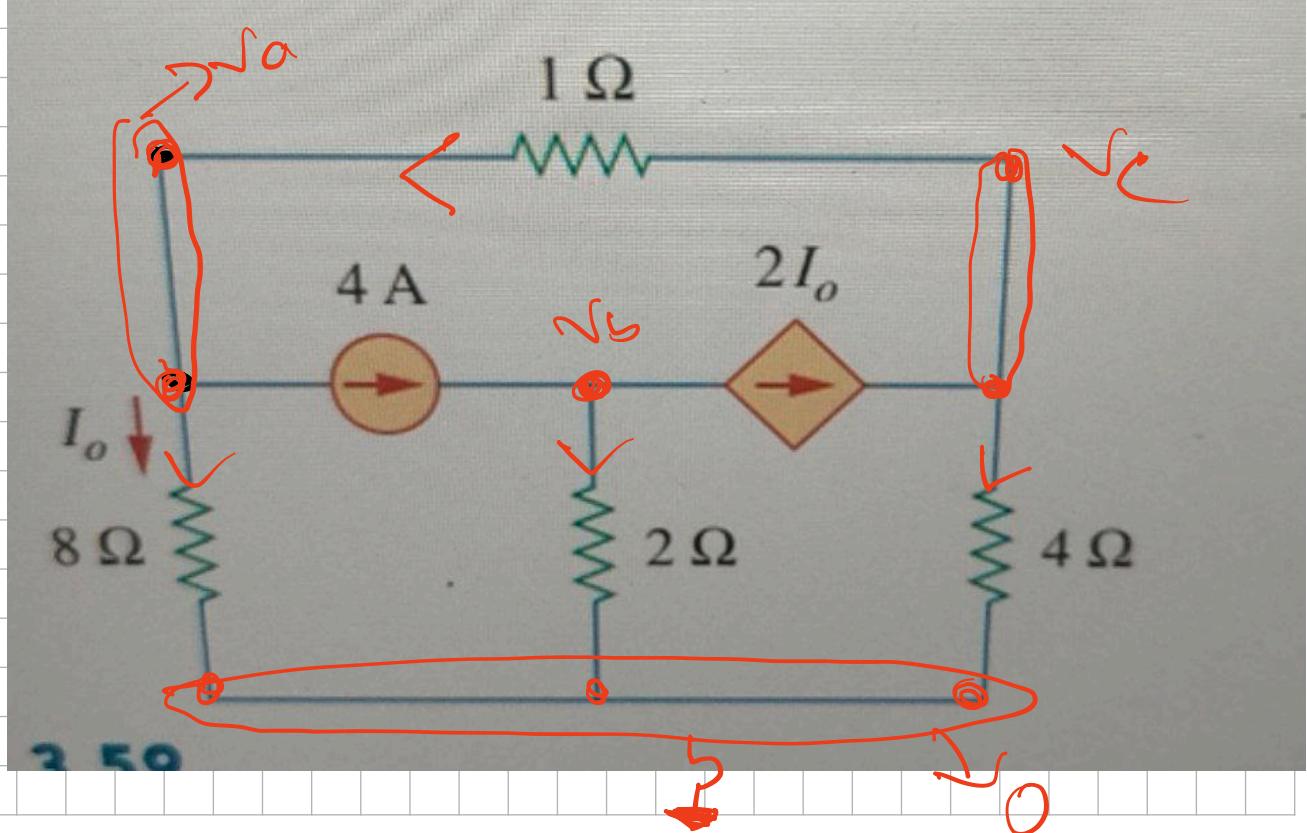

KCL at V_a :

$$\frac{V_c - V_a}{1} = \frac{V_a - 0}{8} + 9$$

$$\Rightarrow 8V_c - 8V_a = V_a + 32$$

$$\Rightarrow -9V_a + 8V_c = 32 \quad \text{--- } \textcircled{1}$$

KCL at V_b :

$$\frac{V_b - 0}{2} + 2I_0 = 9$$

$$\Rightarrow V_b + 9I_0 = 8$$

$$\Rightarrow V_b + 9 \times \frac{V_a - 0}{8} = 8$$

$$\Rightarrow V_a + 2V_b = 16 \quad \text{--- } \textcircled{II}$$

KCL at V_c :

$$2I_0' = \frac{V_c - V_a}{1} + \frac{V_c - 0}{9}$$

$$\Rightarrow 2 \times \frac{V_a - 0}{8} = V_c - V_a + \frac{V_c}{9}$$

$$\Rightarrow 2V_a = 8V_c - 8V_a + 2V_c$$

$$\Rightarrow 10V_a - 10V_c = 0$$

\therefore From (i)(ii)(iii) \Rightarrow


$$V_a =$$

$$V_b =$$

$$V_c =$$

$$\therefore f_0 = \frac{V_a}{8}$$

~~A_m~~

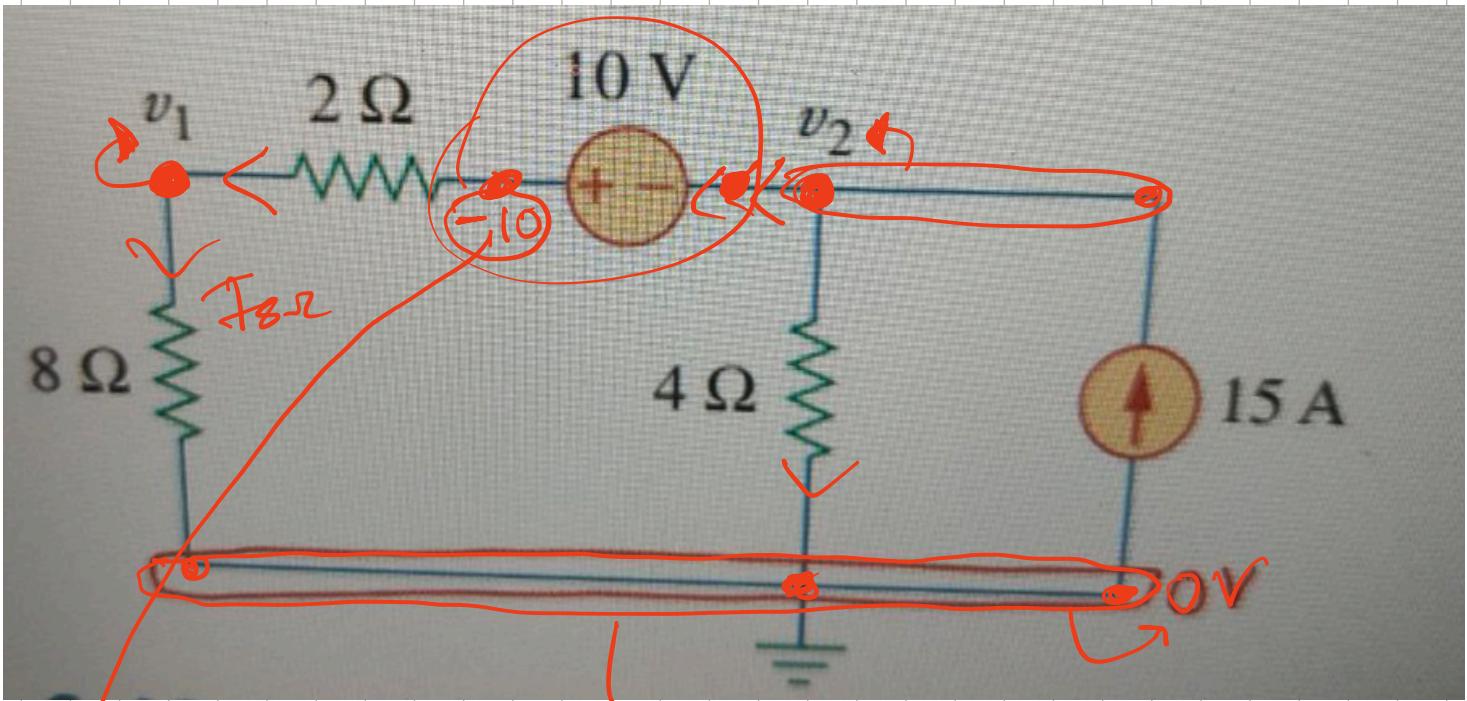

KCL at V_2 :

$$I_5 = \frac{V_2}{9}$$


Ground voltage source
opp. to ground $\rightarrow 10\text{V}$

2nd loop voltage
at ground & 9Ω
series
loop
 $\Sigma V = 0$

$$\Rightarrow 15 = 2 \cdot 5 V_2 + V_2 + 10$$

$$\therefore 3 \cdot 5 V_2 = 40$$

$$\therefore V_2 = 40$$

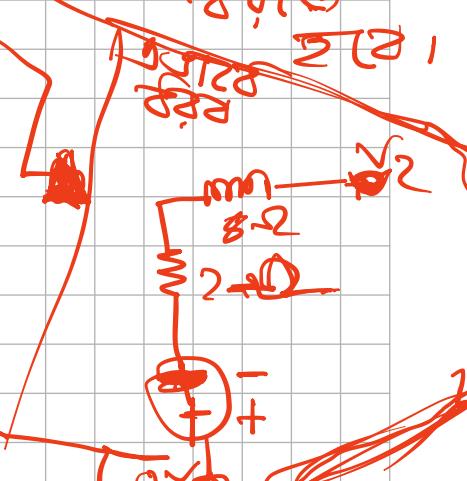

KCL at V_1 : $V_{8\Omega} = V_1 - 0$

$$\begin{aligned} V_1 &= I_{8\Omega} \times 8 \\ &= 5 \times 8 \\ &= 40 \text{V} \end{aligned}$$

$$\begin{aligned} V_{8\Omega} &= V_{2\Omega} = \frac{V_2 - (-10)}{10} \\ &= \frac{40}{10} = 4 \text{A} \end{aligned}$$


[Issue: Voltage source \rightarrow Source \rightarrow Opposite voltage point than V_1 .]

\rightarrow type Math solution

voltage source from ground \rightarrow
move voltage \rightarrow solve


opposite \rightarrow short

series \rightarrow open

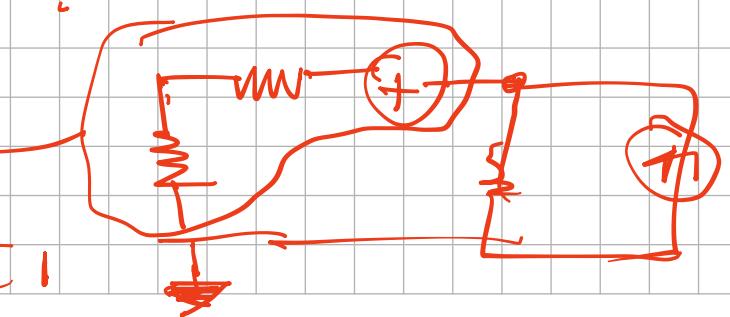

Open circuit Reversing end voltage
Source V_{TCO} Ground at V_{TCO}

Fig 1. O.C.T

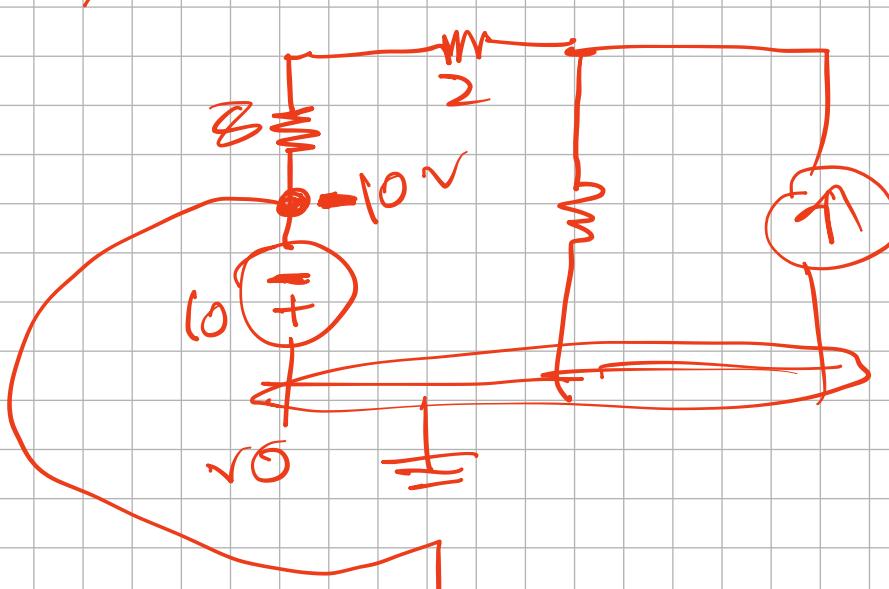

V_{OC}
Voltage
at V_{OC}
is 20V.

At node 2 node V_{TCO} connect

$$\text{Voltage across } R_2 = -10 - 0 = -10V$$

Open node voltage value

Circuit Nodal or mesh method

Method,